

CSE 260M / ESE 260

Intro. To Digital Logic & Computer Design


Bill Siever
&
Michael Hall

Modules 1-4A

Module 1

Binary

- Counting / bases
 - (Unsigned) Binary: 0, 1, 10, 11, ...
 - One-to-one correspondence with natural numbers



Decimal:	0	1	2	3	4	5	6	7
Binary:	000	001	010	011	100	101	110	111

Place Value: Base b (to decimal)

Digits	D2	D1	D0
Place Value	b^2	b^1	b^0
Place Value In terms of Base	$D2 \cdot b^2$	$D1 \cdot b^1$	$D0 \cdot b^0$

Highlights

- Different bases have different strengths (for this course & computing)
 - Decimal: Human's "first learned base" (typically)
 - Binary: On/off notation is convenient for building machines
 - Hexadecimal: More human friendly than binary, but direct conversion to/from binary
 - Arithmetic in all (these) bases can be thought about based number lines (Ex: Addition of positives is moving to the right on the number line)

Highlights


- Often used for “encoding” — using a binary number to represent some concept
 - Ex: State Encodings represent the concept of a state machine’s state. (Numeric value, but numeric value may not be significant)
 - Ex: ASCII (encoding English letters)

Negatives

- We've focused on numbers with a fixed width (i.e., n digits)
- Multiple representations
 - Sign/Magnitude: Like the notion of the “-“ in decimal representations
 - Two's Complement: Divide the number line into non-neg and negs. Convenient:
 - Can use modified place-value rules to do human-friendly conversions.
 - Can use same rules for addition as with unsigned

Dividing the Line

- Split the line in half, like we've already done.
- How can we identify if a binary number is positive or negative?
 - Ex: 010? Or 110?

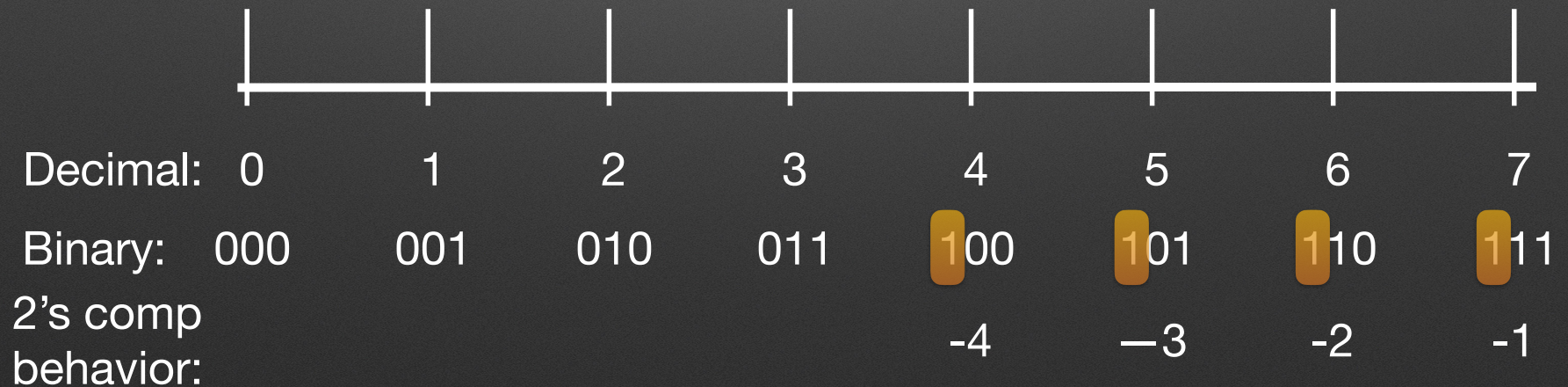

Module 2

Boolean Algebra

- Rules / processes to manipulate true/false statements and values
- Formal Algebraic Rules
(partly from from George Boole's "The Mathematical Analysis of Logic")
 - Basic operations: AND, OR, Not
- Doesn't represent notion of time or real-world behavior

Boolean Algebra

Table 2.1 Axioms of Boolean algebra

	Axiom		Dual	Name
A1	$B = 0$ if $B \neq 1$	A1'	$B = 1$ if $B \neq 0$	Binary field
A2	$\bar{0} = 1$	A2'	$\bar{1} = 0$	NOT
A3	$0 \bullet 0 = 0$	A3'	$1 + 1 = 1$	AND/OR
A4	$1 \bullet 1 = 1$	A4'	$0 + 0 = 0$	AND/OR
A5	$0 \bullet 1 = 1 \bullet 0 = 0$	A5'	$1 + 0 = 0 + 1 = 1$	AND/OR

Boolean Algebra

Table 2.2 Boolean theorems of one variable

	Theorem		Dual	Name
T1	$B \bullet 1 = B$	T1'	$B + 0 = B$	Identity
T2	$B \bullet 0 = 0$	T2'	$B + 1 = 1$	Null Element
T3	$B \bullet B = B$	T3'	$B + B = B$	Idempotency
T4		$\overline{\overline{B}} = B$		Involution
T5	$B \bullet \overline{B} = 0$	T5'	$B + \overline{B} = 1$	Complements

Boolean Algebra

Table 2.3 Boolean theorems of several variables

	Theorem		Dual	Name
T6	$B \cdot C = C \cdot B$	T6'	$B + C = C + B$	Commutativity
T7	$(B \cdot C) \cdot D = B \cdot (C \cdot D)$	T7'	$(B + C) + D = B + (C + D)$	Associativity
T8	$(B \cdot C) + (B \cdot D) = B \cdot (C + D)$	T8'	$(B + C) \cdot (B + D) = B + (C \cdot D)$	Distributivity
T9	$B \cdot (B + C) = B$	T9'	$B + (B \cdot C) = B$	Covering
T10	$(B \cdot C) + (B \cdot \bar{C}) = B$	T10'	$(B + C) \cdot (B + \bar{C}) = B$	Combining
T11	$(B \cdot C) + (\bar{B} \cdot D) + (C \cdot D)$ $= (B \cdot C) + (\bar{B} \cdot D)$	T11'	$(B + C) \cdot (\bar{B} + D) \cdot (C + D)$ $= (B + C) \cdot (\bar{B} + D)$	Consensus
T12	$\overline{B_0 \cdot B_1 \cdot B_2 \dots}$ $= (\bar{B}_0 + \bar{B}_1 + \bar{B}_2 \dots)$	T12'	$\overline{B_0 + B_1 + B_2 \dots}$ $= (\bar{B}_0 \cdot \bar{B}_1 \cdot \bar{B}_2 \dots)$	De Morgan's Theorem

Tables & Truth

- Truth tables: Provide full behavioral description of inputs/outputs
- Common Digital Logic representations:
 - AND via “multiplication”
 - OR via “addition”
- Why? Order of operations is familiar
- Result: A “product term” is an AND expression


Tables & Truth

- **Minterm:**
Product term that includes all input variables once (possibly with a negation)
 - Corresponds to “Selecting a row” of a truth table
- **Canonical Sum-of-Products form:** Sum (OR) term of all the Minterms for an output
- **Look-up-table (LUT):** Idea of “looking up” a set of inputs in a truth table to determine the output

Karnaugh Maps

- Convenient visual tool for a type of optimization
 - Allows easily combining terms
 - Limited to ~4 variables (typically)
 - If possible, reduces width of AND gates (smaller product terms) and number of OR terms (smaller sum)

Digital Machines

 


- Schematic symbols
 - “Schematic Capture” : Converting design to digital formats (like creating a circuit diagram in JLS)

Machines introduce practical concerns

- How fast/slow is it?
- How much space does it take?
- How much power does it require? / How much does it cost to operate?
- How much does it cost to construct?
- Leads to: How do different implementations compare?
and “What is best”? (Best for what?)


Module 3
Beyond Combinational Logic
(Beyond things that can be simple tables)

SR Latch: A way to store a value!

 

D-Latch: A better way to store data


- Start with SR Latch

 

- Describe Desired Behavior (of output, Q)
- Just combinational logic
- Reset = Clock * /Data
Set = Clock * Data

CLOCK	DATA	Q
0	0	Q_{prev}
0	1	Q_{prev}
1	0	RESET
1	1	SET

D-Latch


 


D-Latch

- “Latches on” to last data value when clock goes low
 - Is sensitive to the level of the clock
 - Is “transparent” when the clock is high
- A bit inconvenient


D Flip-Flop: More precision

 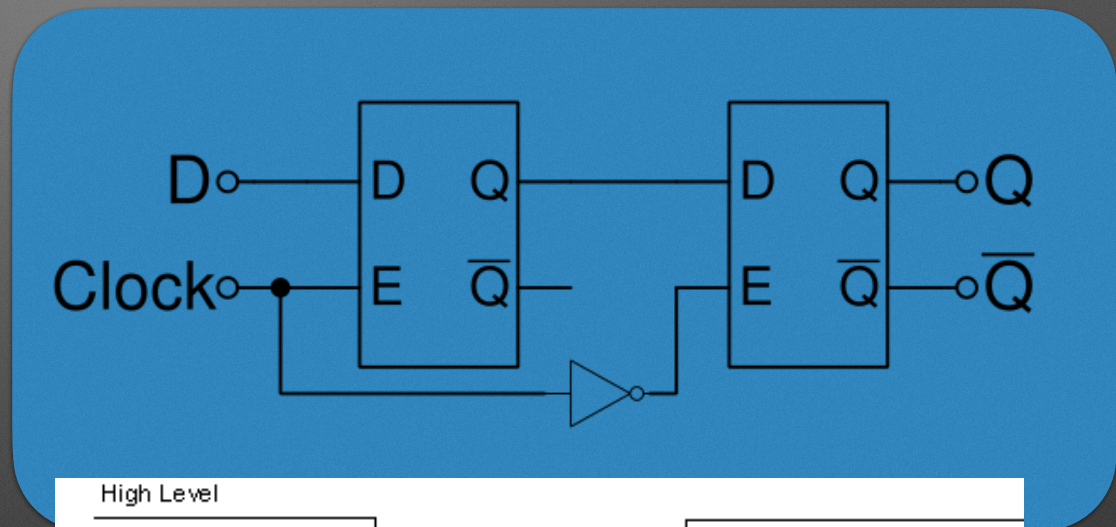- Combines two D-latches using opposite levels
- Results in behavior that is *edge sensitive*: Very precise



Synchronous Sequential Circuits

 - *Synchronized* by a clock
 - Utilize D Flop Flops and combinational logic
 - Clock can ensures proper behavior




(Deterministic) Finite State Machines


- Concept that can be used for many practical problems
 - States: The current “condition” of the machine
(Requiring some concept of current location)
 - Arc: Describe why/when to change states (based on inputs)
 - Outputs: Based on state and input (latter in Mealy machines)
 - Our implementations: Clock controls timing of when states may change

State Machines

 - Just combine prior ideas
 - Binary encoding / State table: Uses binary encoding to represent state
 - State tables: Truth table that captures the “arcs”
 - Output tables: Truth table that captures how outputs behave
- All those are simple combinational logic concepts:
 - Can be represented with equations
 - Can be built using gates
 - Specific design can be depicted with gate-level schematic




FSM: Moore Machine Structure

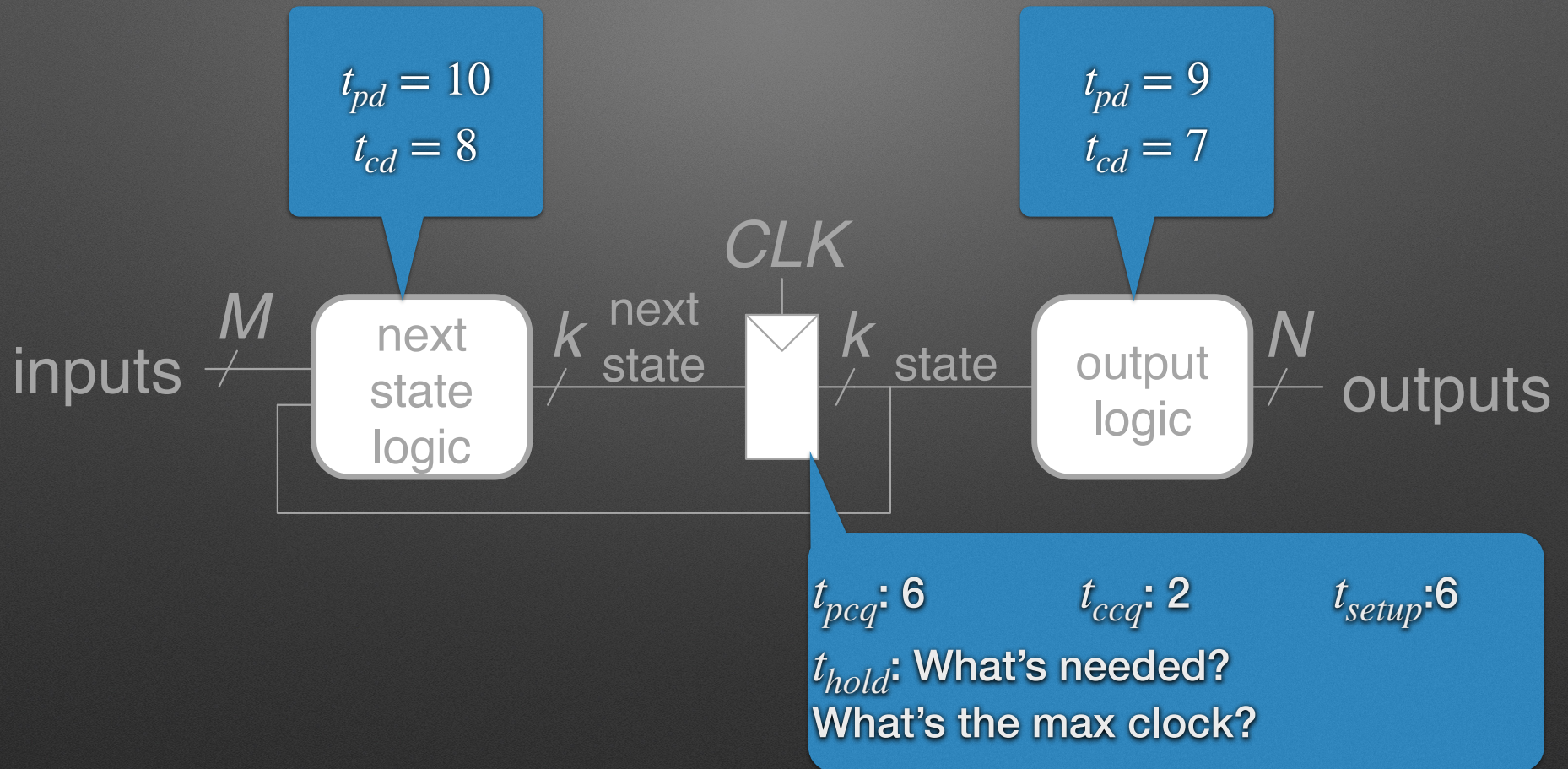

Dff Time Parameters

- t_{pcq} : Propagation delay from Clock to Q (pcq)
- t_{ccq} : Contamination delay from C to Q (ccq)
- t_{setup} : Setup time (for d before clock)
- t_{hold} : Hold time (for d after clock)

 

Module 4


Hardware Description Languages (HDLs)

- Specifies logic function only
- Computer-aided design (CAD) tool produces or synthesizes the optimized gates
- Most commercial designs built using HDLs

HDL


- A HDL is NOT a computer program!

(System) Verilog Module Example

 


```
module example(input logic a, b, c,  
               output logic y);  
    // module body goes here  
endmodule
```

 Input & Output
are like the Pins
On chips or in
JLS



HDL: Structural (Verilog)

 

```
module nand3(input logic a, b, c
             output logic y);
    logic n1; // internal signal

    and my_and(n1, a, b, c); // instance of and3
    not my_inverter(y, n1); // instance of inv
endmodule
```

HDL: Behavioral (Verilog)

```
module nand3(input  logic a, b, c
             output logic y);
    assign y = ~(a & b & c);
endmodule
```